

GATE QUESTION

Avinash Bhargav Reddy

February 1, 2024

1. In the circuit shown, what are the values of F for $EN = 0$ and $EN = 1$, respectively?

(GATE-EC2019,14)

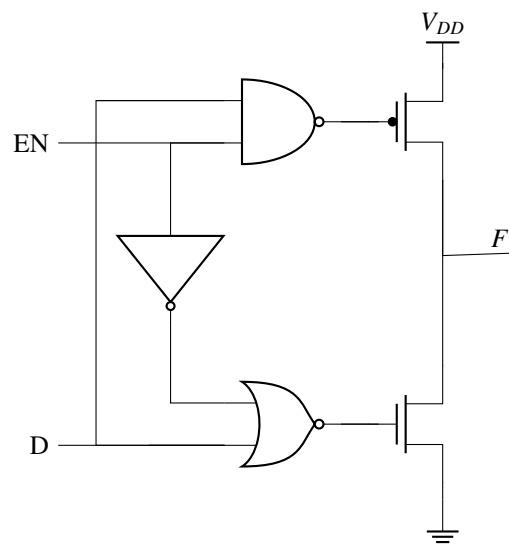


Figure 1: Circuit diagram

1. 0 and D
2. $Hi - Z$ and D
3. 0 and 1
4. $Hi - Z$ and \bar{D}